

Fall 2022

- Home
- Announcements
- Assignments
- Discussions
- Grades
- People
- Pages
- Files
- Syllabus
- Quizzes**
- Modules
- Collaborations
- Chat
- Piazza
- Office 365
- TurningPoint
- CIOs
- Badges
- Ed Discussion
- Microsoft Teams meetings
- Zoom
- GT Student Resources
- Media Gallery

SD2 Response Page

Due Sep 20 at 11:59pm Points 21 Questions 21 Time Limit None
Allowed Attempts Unlimited

Instructions

For all answers just enter the number *without* the units. (I'm trying a different answer bot).
The quiz allows multiple attempts, but (unfortunately), it forgets your previous correct answers on successive attempts. We recommend recording your answers so you can re-use the correct ones.

Take the Quiz Again

Last Attempt Details:

Time: 3 minutes
Current Score: 21 out of 21
Kept Score: 21 out of 21

3 Attempts so far
[View Previous Attempts](#)
Unlimited Attempts


[Take the Quiz Again](#)

(Will keep the highest of all your scores)

Correct answers are hidden.

Score for this attempt: **21** out of 21
Submitted Sep 15 at 9:57pm
This attempt took 3 minutes.


Question 1 1 / 1 pts

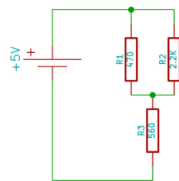

Resistors: Equivalent resistance of these three resistors? (no units, just the number)

947.2659


Question 2 1 / 1 pts

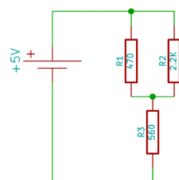

Resistors: What is the total current through this resistor network? (just the number in milliamps, such a "19.2")

5.278


Question 3 1 / 1 pts

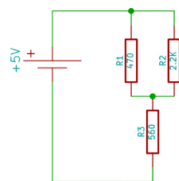

Resistors: What is the current flow through R3? (just the number in milliamps)

5.278

Question 4 1 / 1 pts

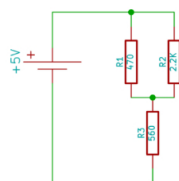


Resistors: What is the voltage across R3? (just the number in volts)

Resistors: What is the voltage across R1? (just the number in volts)

2.956

Question 5

1 / 1 pts

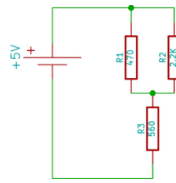


Resistors: What is the voltage across R1? (just the number in volts)

2.0443

Question 6

1 / 1 pts

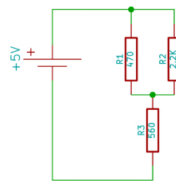


Resistors: What is the voltage across R2? (just the number in volts)

2.0443

Question 7

1 / 1 pts

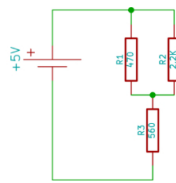


Resistors: What is the current across R1? (just the number in milliamps)

4.3496

Question 8

1 / 1 pts

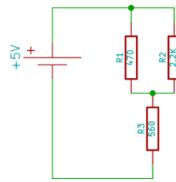


Resistors: What is the current across R2? (just the number in milliamps)

0.929

Question 9

1 / 1 pts

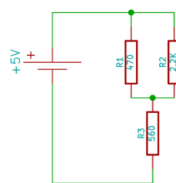

Resistors: Color code for R1: yellow violet brown

Select from black, brown, red, orange, yellow, green, blue, violet, grey, white.

Answer 1:

yellow

Answer 2:


violet

Answer 3:

brown

Question 10

1 / 1 pts

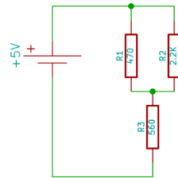

Resistors: Color code for R2: red red red

Select from black, brown, red, orange, yellow, green, blue, violet, grey, white.

Answer 1:

red

Answer 2:


red

Answer 3:

red

Question 11

1 / 1 pts

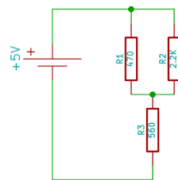

Resistors: Color code for R3: green blue brown

Select from black, brown, red, orange, yellow, green, blue, violet, grey, white.

Answer 1:

green

Answer 2:

blue


Answer 3:

brown

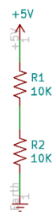Question 12

1 / 1 pts

Build the below circuit from the resistors in your kit. Power it from your Arduino.




Two resistors in series: What is the voltage at top of R1? _____ volts. (Just the number.)

5

Question 13

1 / 1 pts

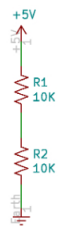

Two resistors in series: What is the voltage at connection between R1 and R2?
 volts. (Just the number.)

Question 14

1 / 1 pts



Two resistors in series: What is the voltage at bottom of R2? volts. (Just the number.)

Question 15

1 / 1 pts




Two resistors in series: What is the total current through the two resistors in milliamps?

(Find the total resistance and calculate the current with ohms law.)

Question 16

1 / 1 pts

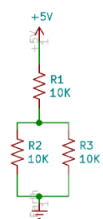


Three resistors: What is the voltage at the top of the network?

Question 17

1 / 1 pts




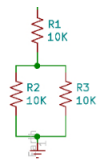

Three resistors: What is the voltage at the middle of the network?

Question 18


1 / 1 pts

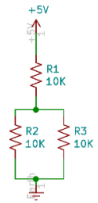

Three resistors: What is the voltage at the bottom of the network?

Question 19


1 / 1 pts

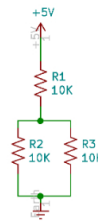

Three resistors: What is the total current through the network? (Answer in milliamps.)

Question 20

1 / 1 pts

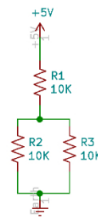


How much power in milliwatts does this voltage divider use?

(Remember the power equation $P = I V$)

Question 21

1 / 1 pts

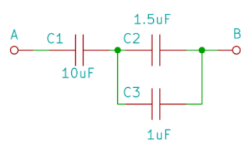

What is the total capacitance between point A and B in this circuit? (in uF or microfarads)

